

Electronic Circuits

Prof. Nizamettin AYDIN

naydin@yildiz.edu.tr

<http://www.yildiz.edu.tr/~naydin>

Dr. Gökhan Bilgin

gokhanb@ce.yildiz.edu.tr

1


Transistor Construction

There are two types of transistors:

- *pn*p
- *np*n

The terminals are labeled:

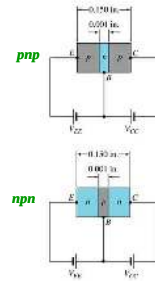- E - **E**mitter
- B - **B**ase
- C - **C**ollector




2

Transistor Operation

With the external sources, V_{EE} and V_{CC} , connected as shown:

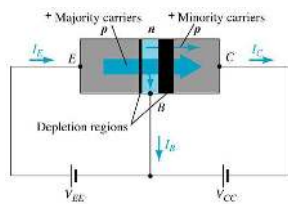- The emitter-base junction is forward biased
- The base-collector junction is reverse biased



3


Currents in a Transistor

Emitter current is the sum of the collector and base currents:

$$I_E = I_C + I_B$$


The collector current is comprised of two currents:
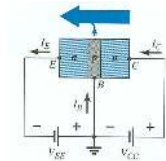
$$I_C = I_{C_{\text{majority}}} + I_{C_{\text{minority}}}$$



4

Common-Base Configuration

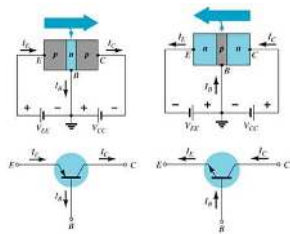


The base is common to both input (emitter-base) and output (collector-base) of the transistor.

5

Common-Base Amplifier

Input Characteristics

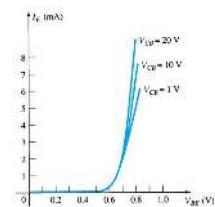This curve shows the relationship between of input current (I_E) to input voltage (V_{BE}) for three output voltage (V_{CB}) levels.




6

Common-Base Amplifier

Output Characteristics

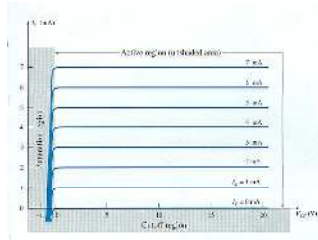This graph demonstrates the output current (I_C) to an output voltage (V_{CB}) for various levels of input current (I_E).



7

Operating Regions

- **Active** – Operating range of the amplifier.
- **Cutoff** – The amplifier is basically off. There is voltage, but little current.
- **Saturation** – The amplifier is full on. There is current, but little voltage.

8

Approximations

Emitter and collector currents:

$$I_C \approx I_E$$

Base-emitter voltage:

$$V_{BE} = 0.7 \text{ V (for Silicon)}$$

9

Alpha (α)

Alpha (α) is the ratio of I_C to I_E :

$$\alpha_{dc} = \frac{I_C}{I_E}$$

Ideally: $\alpha = 1$


In reality: α is between 0.9 and 0.998

Alpha (α) in the AC mode:

$$\alpha_{ac} = \frac{\Delta I_C}{\Delta I_E}$$

10

Transistor Amplification

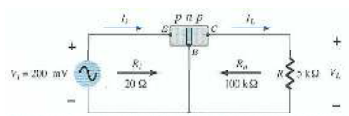

Currents and Voltages:

$$I_E = I_i = \frac{V_i}{R_i} = \frac{200 \text{ mV}}{20 \Omega} = 10 \text{ mA}$$

$$I_C \approx I_E$$

$$I_L \approx I_i = 10 \text{ mA}$$

$$V_L = I_L R = (10 \text{ mA})(5 \text{ k}\Omega) = 50 \text{ V}$$

Voltage Gain:


$$A_v = \frac{V_L}{V_i} = \frac{50 \text{ V}}{200 \text{ mV}} = 250$$

11

Common-Emitter Configuration


The emitter is common to both input (base-emitter) and output (collector-emitter).

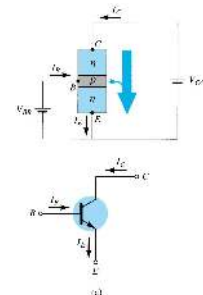The input is on the base and the output is on the collector.



12

Common-Emitter Characteristics

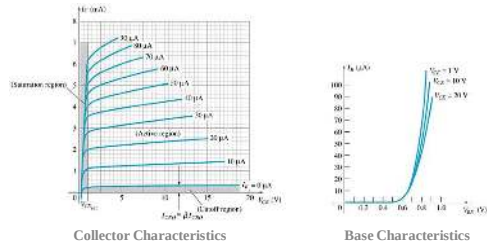

13

Common-Emitter Amplifier Currents

Ideal Currents

$$I_E = I_C + I_B$$

$$I_C = \alpha I_E$$

Actual Currents

$$I_C = \alpha I_E + I_{CBO} \quad \text{where } I_{CBO} = \text{minority collector current}$$

I_{CBO} is usually so small that it can be ignored, except in high power transistors and in high temperature environments.

When $I_B = 0 \mu A$ the transistor is in cutoff, but there is some minority current flowing called I_{CEO} .

$$I_{CEO} = \frac{I_{CBO}}{1 - \alpha} \quad I_B = 0 \mu A$$

14

Beta (β)

β represents the amplification factor of a transistor. (β is sometimes referred to as h_{fe} , a term used in transistor modeling calculations)

In DC mode:

$$\beta_{dc} = \frac{I_C}{I_B}$$

In AC mode:

$$\beta_{ac} = \frac{\Delta I_C}{\Delta I_B} \bigg|_{V_{CE} = \text{constant}}$$


15

Beta (β)

Determining β from a Graph

$$\begin{aligned} \beta_{AC} &= \frac{(3.2 \text{ mA} - 2.2 \text{ mA})}{(30 \mu A - 20 \mu A)} \\ &= \frac{1 \text{ mA}}{10 \mu A} \bigg|_{V_{CE} = 7.5} \\ &= 100 \end{aligned}$$

$$\begin{aligned} \beta_{DC} &= \frac{2.7 \text{ mA}}{25 \mu A} \bigg|_{V_{CE} = 7.5} \\ &= 108 \end{aligned}$$

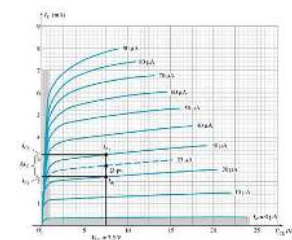

16

Beta (β)

Relationship between amplification factors β and α

$$\alpha = \frac{\beta}{\beta + 1} \quad \beta = \frac{\alpha}{\alpha - 1}$$


Relationship Between Currents

$$I_C = \beta I_B \quad I_E = (\beta + 1) I_B$$

17

Common-Collector Configuration

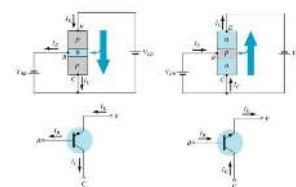
The input is on the base and the output is on the emitter.



18

Common-Collector Configuration

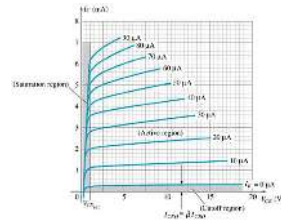The characteristics are similar to those of the common-emitter configuration, except the vertical axis is I_E .




19

Operating Limits for Each Configuration

V_{CE} is at maximum and I_C is at minimum ($I_{C_{max}} = I_{CEO}$) in the cutoff region.

I_C is at maximum and V_{CE} is at minimum ($V_{CE\max} = V_{CEsat} = V_{CE0}$) in the saturation region.

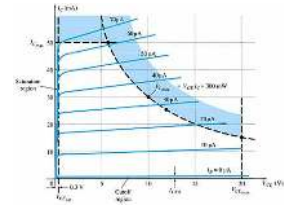The transistor operates in the active region between saturation and cutoff.



20

Power Dissipation

Common-base:

$$P_{Cmax} = V_{CB}I_C$$

Common-emitter:

$$P_{Cmax} = V_{CE} I_C$$

Common-collector:

$$P_{Cmax} = V_{CE} I_E$$

21

Transistor Specification Sheet

MAXIMUM RATINGS			
Rating	Symbol	204(2)	Unit
Collector-Emitter Voltage	V_{CE}	30	Vdc
Collector-Base Voltage	V_{CB}	30	Vdc
Emitter-Base Voltage	V_{EB}	3.0	Vdc
Collector Current - Continuous	I_C	210	mA dc
Total Device Dissipation $T_A = 25^\circ\text{C}$	P_D	625	mW
Derate above 25°C		3.1	mW/ $^\circ\text{C}$
Operating and Storage Junction Temperature Range	T_A, T_{stg}	-55 to +150	$^\circ\text{C}$

THERMAL CHARACTERISTICS			
Characteristic	Symbol	Max	Unit
Thermal Resistance, Junction-to-Case	$R_{\theta JA}$	33.3	$^\circ\text{C/W}$
Thermal Resistance, Junction-to-Ambient	$R_{\theta JA}$	200	$^\circ\text{C/W}$



22


Transistor Specification Sheet

[illegible]

23

Transistor Testing

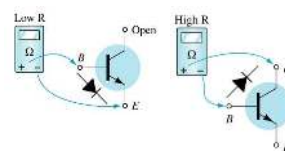- **Curve Tracer**
Provides a graph of the characteristic curves.
- **DMM**
Some DMMs measure β_{DC} or h_{FE} .
- **Ohmmeter**



24

Transistor Terminal Identification

Transistor Terminal Identification